

Juan Rodríguez Archilla


FZ, A1, G1

Zom \rightarrow 1V

$\Im_m(V)$

$$\vec{V}_R = 3,41V \angle 0^\circ$$

$$\vec{V}_C = 5,23V \angle -50^\circ$$

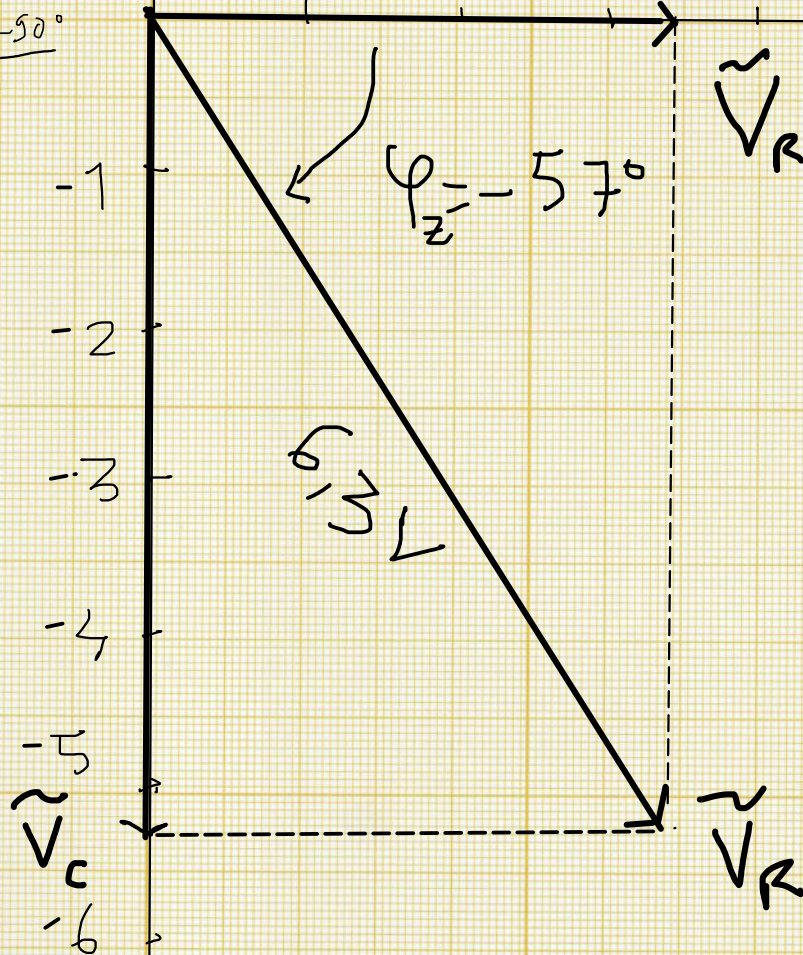

	$ \vec{V} (V)$	$\varphi_z (V)$
Gráf.	6,3	-57°
Exp.	6,31	$-56,2^\circ$